


Name:

Date:


Discharging Capacitor (RC in DC) Lab

Purpose:

Charging:

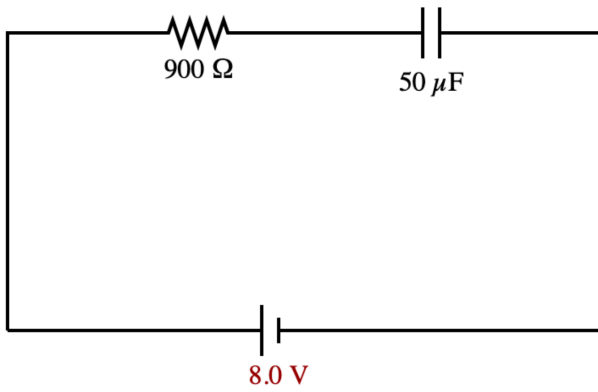

Discharging:

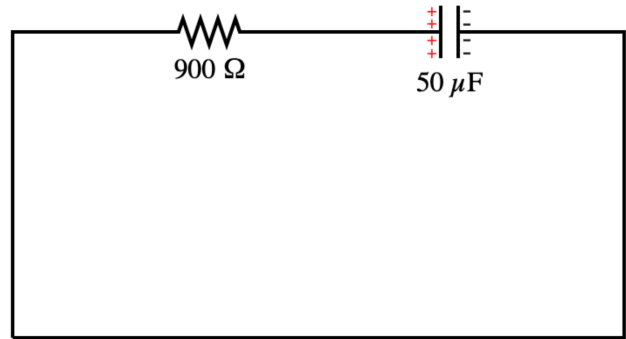

Data:


Discharge Data Through Different Resistors

900 Ω		500 Ω		200 Ω	
t (s)	q (μC)	t (s)	q (μC)	t (s)	q (μC)

Name:

Date:

Graph:

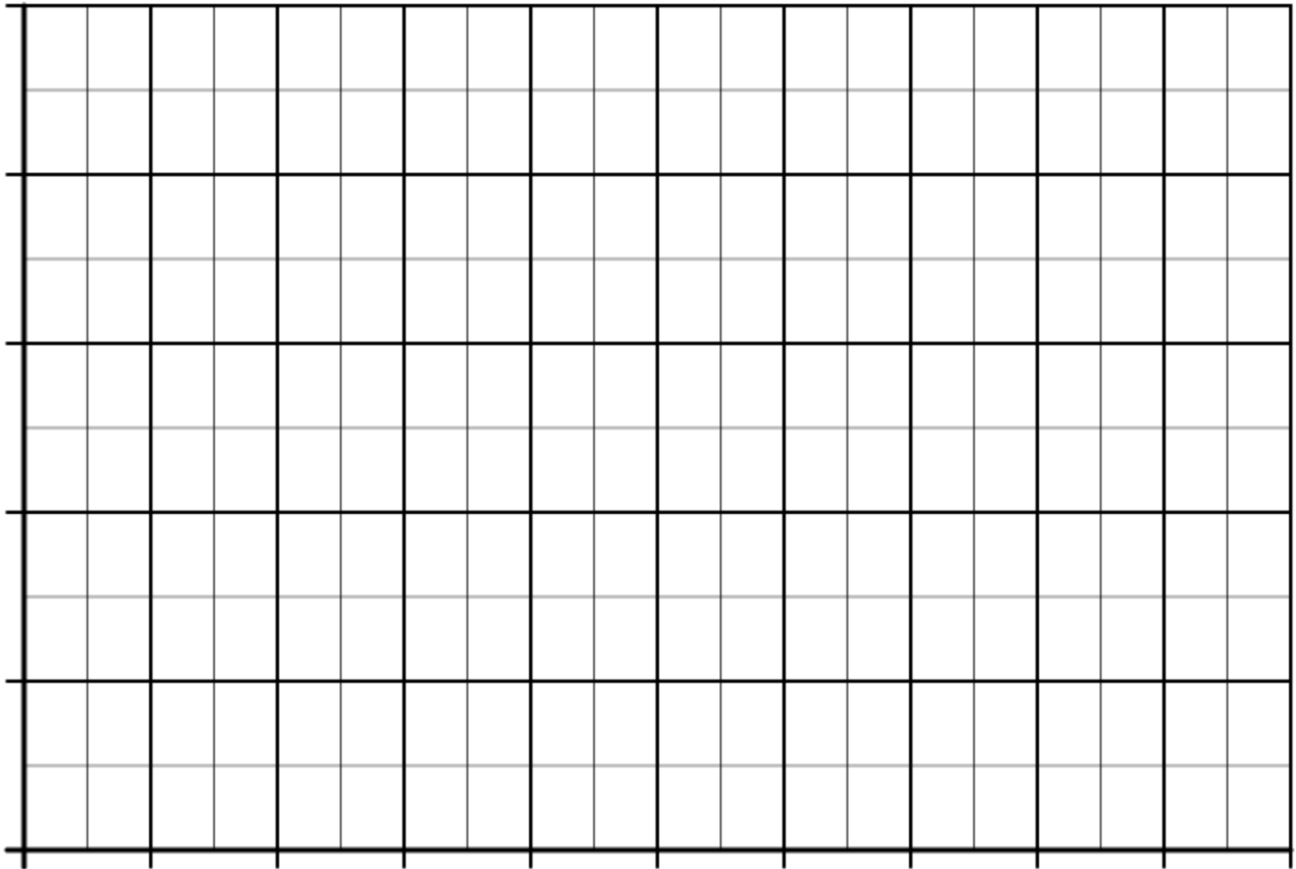

Conclusion: