Name:


Date:

Power of Light Lab

Purpose:

Steps:

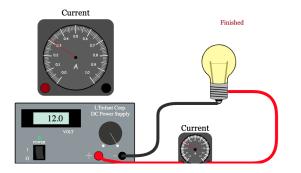Turn on your power supply and then use the dial to adjust the voltage of the supply. Use the voltage and the current to calculate the power. Collect sufficient data to determine the relationship between voltage and power.




Data:

Voltage (V)	Current (A)	Power (W)

Name:

Date:

Graph:

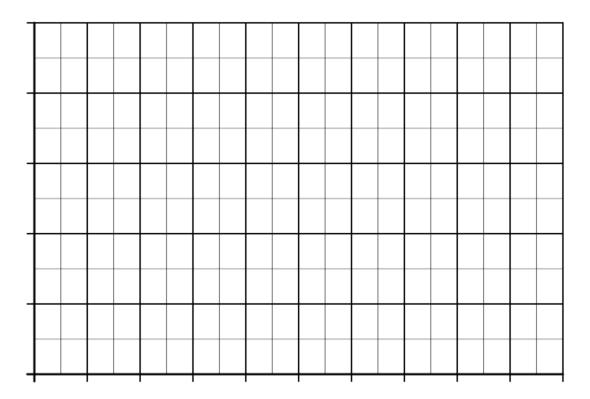

Equation:

Conclusion: